



**Brunel**  
University  
London

重慶郵電大學

CHONGQING UNIVERSITY OF POSTS AND TELECOMMUNICATIONS

# Transistors Sec.1

**Team**

Autumn, 2022

**Module**

EE1616 Electronics

**Workshop**

**Class**

34092102

**Brunel ID**

2161047

**CQUPT ID**

2021215069

**Name**

Xukang Liu

**Tutor**

Zhipeng Wang

## Introduction and aims:

To do some simulates based on **Bipolar Junction Triode (BJT)**.

To determine the transistor's gain and other features from its collector characteristics.

Through this simulation experiment, try to familiar with the characteristics of transistors.

## Task description:

1. Familiar with the theory which we learned before. Understand the typical collector characteristics for a bipolar transistor.
2. Test the characteristic of transistor.  $I_b$  and  $V_{ce}$  as variable, find the characteristic of the curve. Distinguish between saturation region and amplification region.
3. Connect the DC voltage source to collector directly. Draw the circuit diagram and simulate as required. In addition, comments on your results.


## Experiment method:

1. Review the characteristics and the theorem of transistors. Be sure to understand the saturation region and amplification region.
2. Simulate the circuit diagram. Record several groups of data, comments the results. Analysis why is the result like this.

# Result and observations:

## 1. Transistors characteristics testing

### 1.1

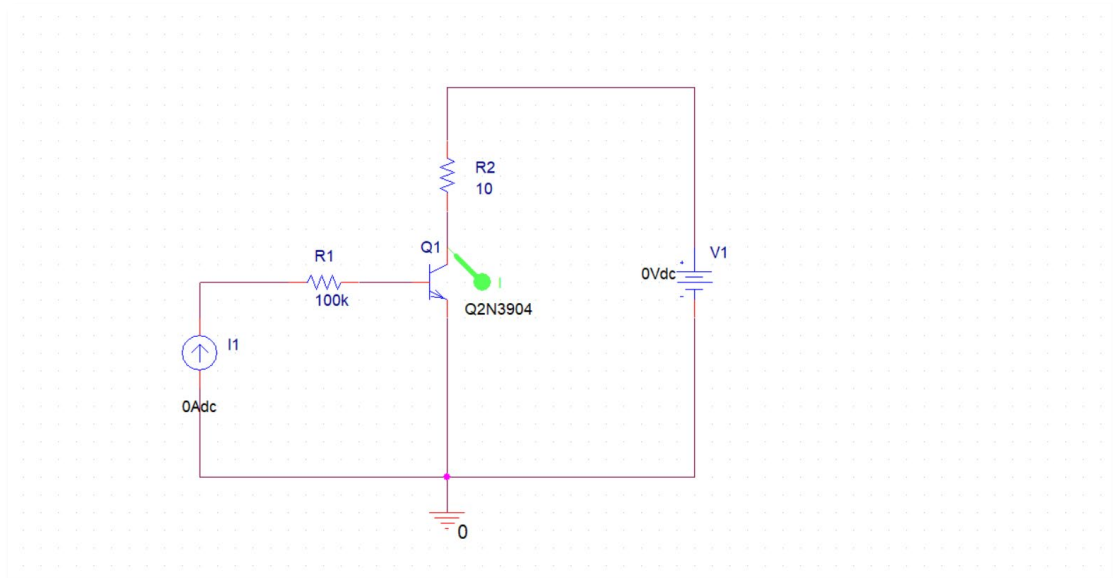


This is the circuit diagram.
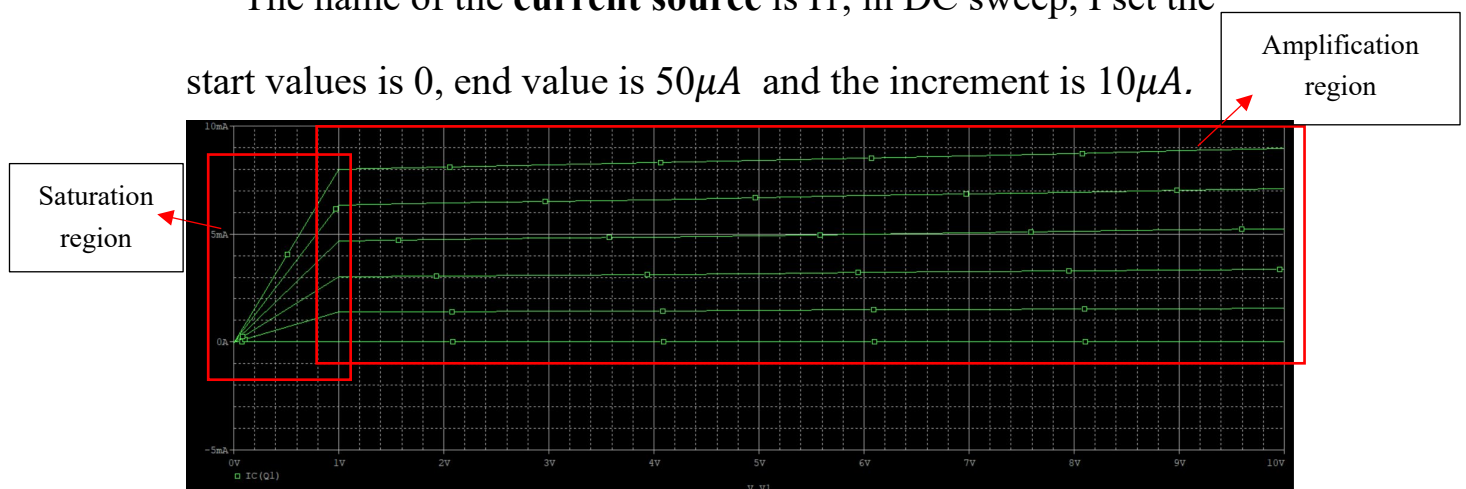
### 1.2

The name of the **voltage source** is V1, in DC sweep, I set the start value is 0, end value is 10 and the increment is 2.

The name of the **current source** is I1, in DC sweep, I set the start values is 0, end value is  $50\mu\text{A}$  and the increment is  $10\mu\text{A}$ .




This is the simulate result. The simulation results are

consistent with the theory



## 1.3

In this part, the power supply is a constant: **10V**. And I need test 3 variables:  $I_b$ ,  $I_c$  and  $V_{ce}$ .

Measure current  $I_c$  against  $I_b$ .

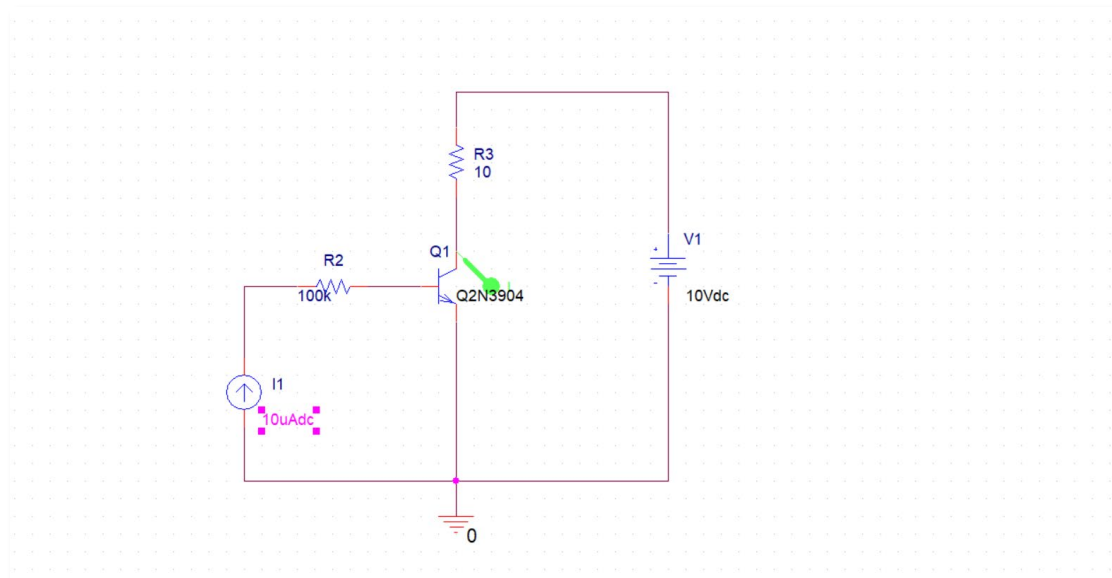

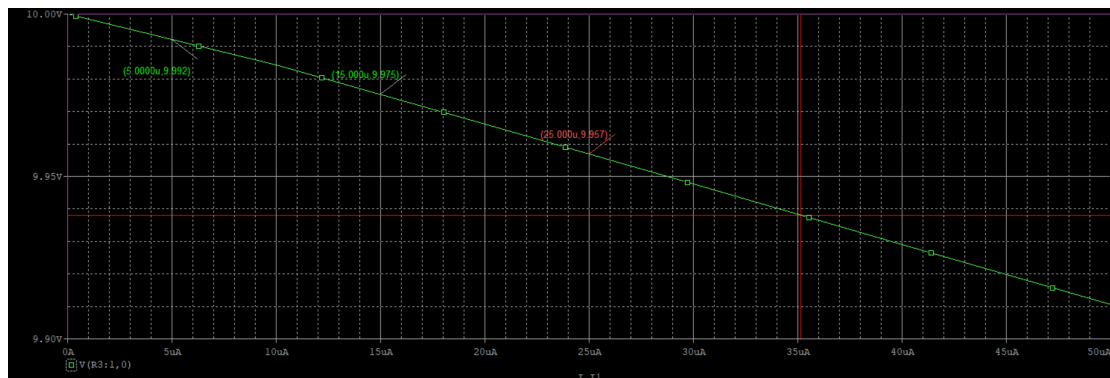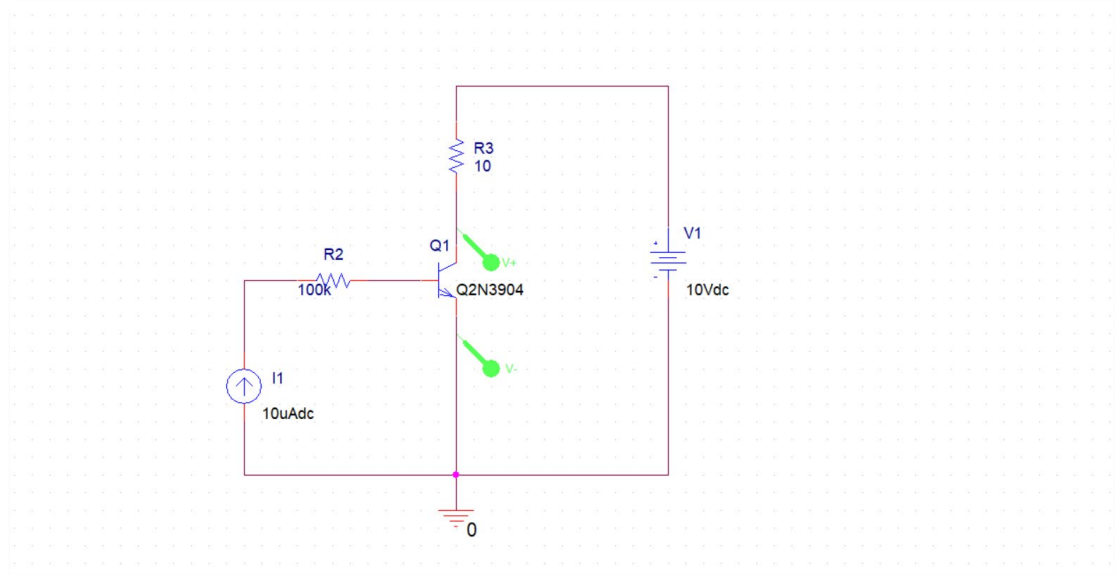Measure voltage  $V_{ce}$  against  $I_b$ .



Finally, I get 3 groups of data.


$I_b$	$I_c$	$V_{ce}$
5uA	0.7779mA	9.92V
15uA	2.4658mA	9.975V
25uA	4.3109mA	9.957V

## 2. Comments on your results

2.1 Obtain experimental answers to Example questions 1 to 3 for your transistor (i.e. determine the collector current, the change in


$I_C$  when  $V_{ce}$  is changed from 2 volts to 10 volts and the current gain of the transistor).

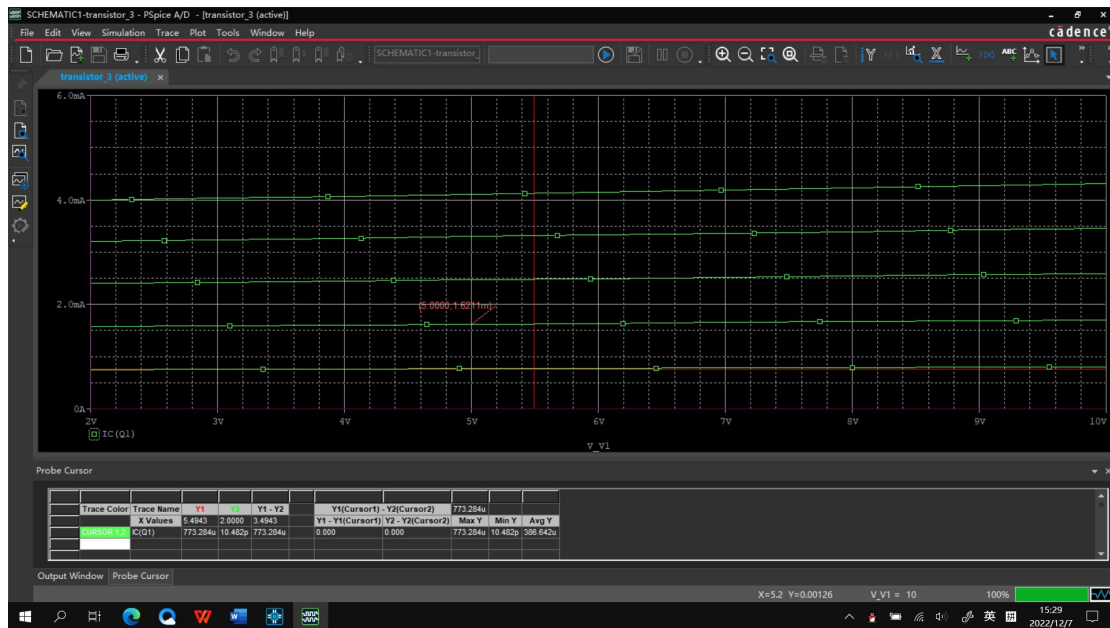- (1) What is the collector current  $I_C$  when the collector-emitter voltage  $V_{ce}$  is 5 volts and the base current  $I_b$  is  $20\text{ }\mu\text{A}$ ?




$I_C$  is 1.6211mA.

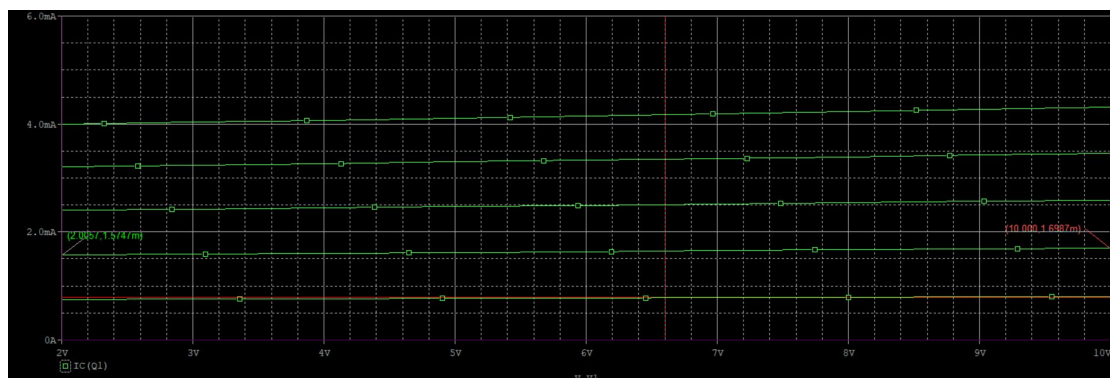- (2) At  $I_b = 20\text{ }\mu\text{A}$ , how much does  $I_C$  change when  $V_{ce}$  is changed from 2 to 10 volts?



$$\Delta I_C = 1.6987 - 1.5747 = 0.124\text{mA}$$

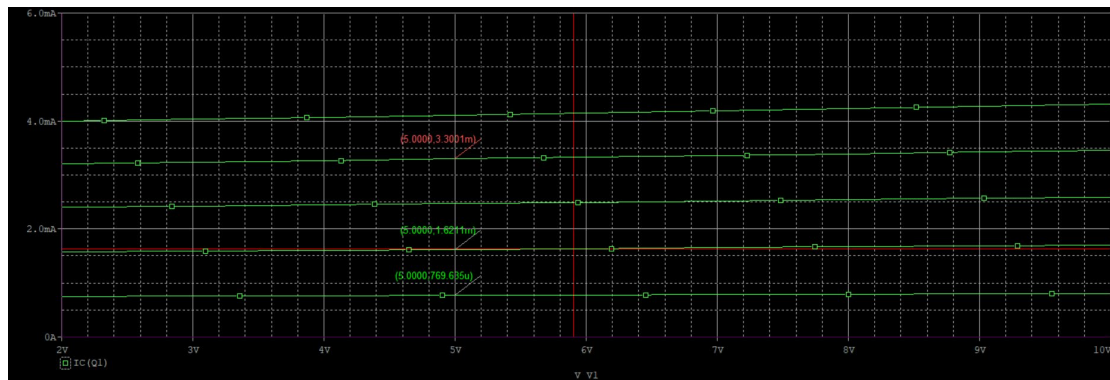(3) What are the current gains ( $I_c/I_b = \beta$ ) at  $V_{ce} = 5$  volts, when  $I_b$  is 10, 20 and 40  $\mu A$ ?



$I_b$  is 10uA,  $I_c$  is 769.635uA  $\beta = 76.97$

$I_b$  is 20uA  $I_c$  is 1.6211mA  $\beta = 77.19$


$I_b$  is 40uA  $I_c$  is 3.3001mA  $\beta = 82.50$

2.2 Now set  $V_{ce}$  to 10 volts and make  $I_c = 5$  mA by varying  $I_b$ .



$I_b = 58.4\mu A$ .

## 2.3

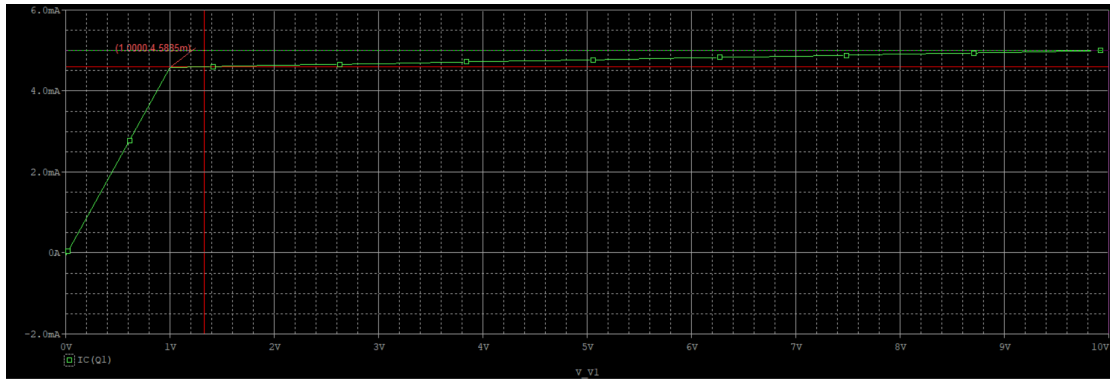


$I_c$  decreased from 4.5885mA to 0.

## 2.4

If the value of  $V_{ce}$  below 1V, the fall of  $I_c$  becomes rapid


## 2.5

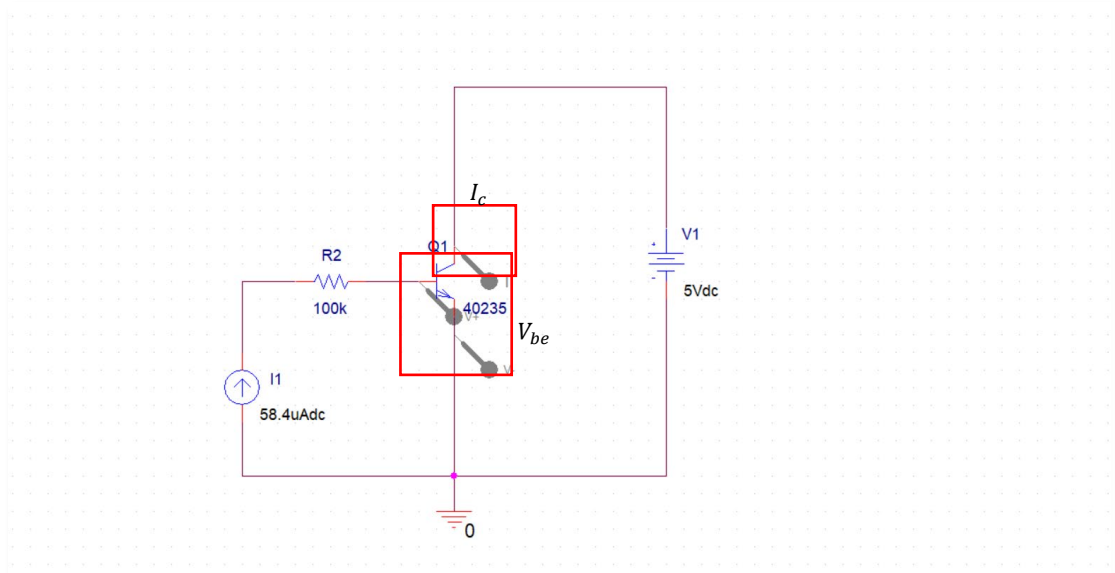




## 2.6

$I_c$  against  $I_b$ :

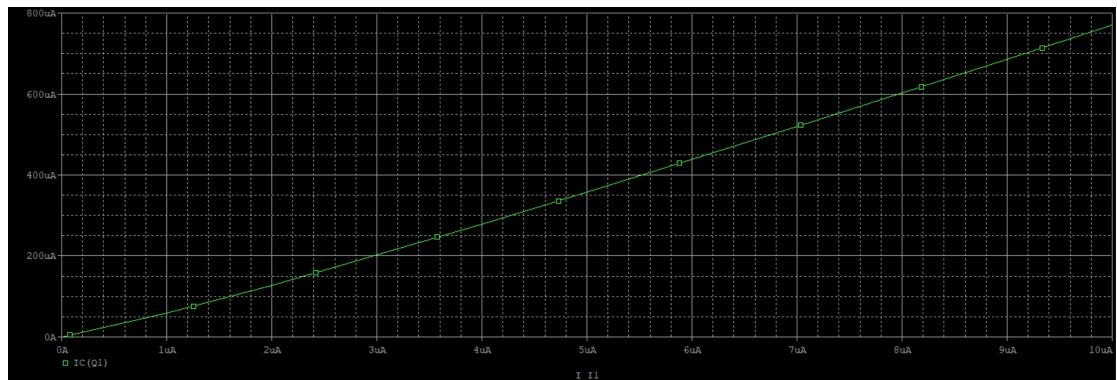


$I_b$  against  $V_{be}$ :

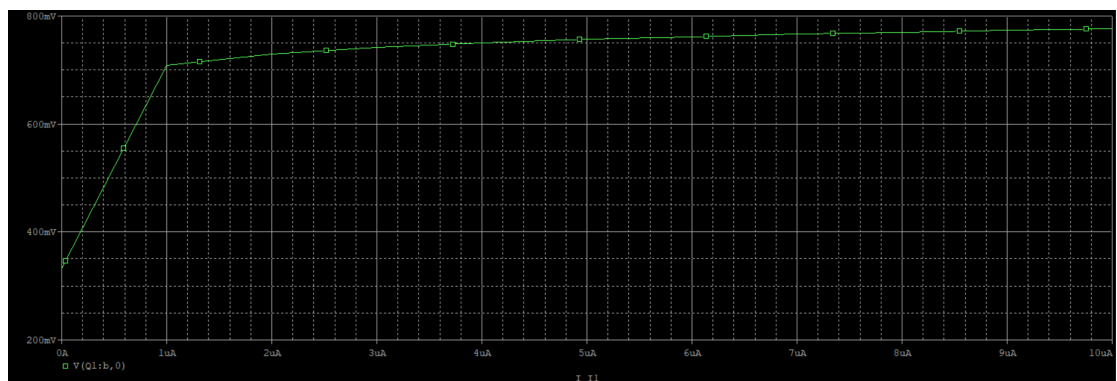
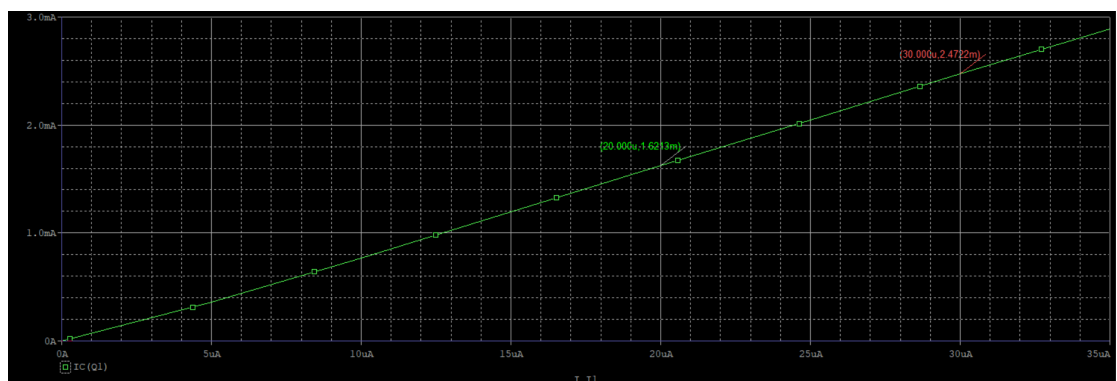
## 2.7

On the premise that the power supply is 5V.



When  $I_b$  is  $20\mu A$ ,  $I_c = 1.6213mA$

When  $I_b$  is  $30\mu A$ ,  $I_c = 2.4722mA$

At  $I_b = 25\mu A$

$$\frac{\Delta I_c}{\Delta I_b} = \frac{(2.4722 - 1.6213) \times 10^3}{30 - 20} = 85.09 = \beta$$

## Conclusion:

In this experiment, I test the characteristic curve of transistor. In the simulation result, I find the saturation region and the amplification region. In addition, I changed some values and simulate the circuit again. This let me know the relationship between  $I_c$ ,  $I_b$ ,  $V_c$ ,  $V_b$ .

